PROJECT NUMBER: 20

MICROPROCESSORS AND INTERFACING DESIGN ASSIGNMENT

"FIRE ALARM SYSTEM"

Submitted by:

1)Saakaar Vashisht (2016A7PS0093P)
2) Saurabh Raj (2016A7PS0094P)
3) Aditi Agarwal (2016A7PS0095P)
4)Gnana Praveen (2016A7PS0096P)

PROBLEM STATEMENT WITH SPECIFICATIONS:

This system checks for abnormal smoke content in a room every 2 seconds. Under abnormal conditions, it throws open 2 doors and 2 windows and opens a valve that releases the gas to put out fire. An alarm is also sounded, this alarm is sounded until smoke level in room drops to an acceptable level. The smoke detection system is made up of 2 smoke sensors placed on the ceiling of the roof. When the smoke level comes back below the danger level, the doors, windows and valves are closed.

ASSUMPTIONS

In order to reduce the design effort as well as to get the simplest design possible using the minimum amount of hardware while meeting all the restrictions specified by our problem statement, we have made the following assumptions:

- 1) The smoke sensors used come with a built in ADC. Such sensors are actually available in market (MQ-2 smoke sensor). It gives high output (1) in case smoke is present near it but gives low output (0) when smoke is not present.
- 2) Abnormal conditions are considered when both the smoke sensors give high output.
- 3)We have used LEDs to simulate the 2 doors, 2 windows, 1 valve and 1 alarm.

Specifications of the problem:

- 1. Two smoke detecting sensors are placed on the ceiling, which detects the smoke content in the room.
- 2. A fire alarm that is sounded when smoke exceeds normal levels.
- 3. Two doors, two windows and valves are controlled by motors.
- 4. The motors and alarms are activated only when **both** the sensors detect an abnormality in smoke levels.

IVT Table:

| Vector No. | Priority | Offset | Use |
|------------|-----------------|--------|-----------------|
| 40h | 1(only one int) | 200h | 8259 calls this |
| | | | interrupt to |
| | | | check for smoke |

DESIGN PROCESS

(A)Components Used:

| Chip Numb er | Quant it | Chip | Purpose |
|--------------------|----------|---|---|
| 8086 | 1 | Microprocessor | Central Processing Unit |
| 8253A | 1 | Programmabl e Interval Timer | Used to generate timing signals |
| 8255A | 1 | Program mable Peripheral Interface | Used to interface ports as input and output for smoke sensors, opening and closing of doors, valves and windows and the sounding of alarm |
| 2732 | 2 | EPROM | R ead o nly Erasable Programmable memory to house code segment |
| 6116 | 2 | RAM | Read and Write Memory to house the segment |
| - | 33 | 2 input OR Gate | Used for Decoding Logic |
| - | 5 | NOT Ga te | Used for Decoding Logic |
| - | 6 | L ED (equivalent to mechanical switch es relay and al arms in c hart) | Simulate doors, windows and valves |
| 74LS3 73 | 3 | 8 bit buffer bi- directional buffers | Buffering address bus |
| 74LS2 45 | 2 | 8 bi t buffer bidirectional buffers | Buffering data bus |
| 74LS2 44 | 2 | Octal Buffers | Creation of Vector number (40h) |

(B) Memory Organization:

Total RAM used by system =

4KB Total ROM used by

system = 8KB RAM chip used

= 6116.

So, size of each RAM chip = 16/8 = 2KB.

Hence, number of 6116 RAM chips required = 4KB/2KB = 2.

EPROM chip used = 2732

So, size of each ROM chip = 32/8 = 4KB.


Hence, number of 2732 EPROM chips required = 8KB/4KB = 2.

Let us consider RAM first.

√ RAM must house the data segment and stack segment.

Starting address of RAM = 00000_H

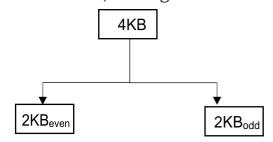System has 4KB RAM. So, Ending address of RAM = 00FFF_H.



 $\textbf{Even Bank of RAM} = 00000_{H}, 00002_{H}, 00004_{H}, 00006_{H}, \dots, 00FFE_{H}.$

 $\textbf{Odd Bank of RAM} = 00001_{H}, 00003_{H}, 00005_{H}, 00007_{H}, \dots, 00FFF_{H}.$

| | A 19 | A_{18} | A ₁₇ | \mathbf{A}_{16} | \mathbf{A}_{15} | \mathbf{A}_{14} | \mathbf{A}_{13} | \mathbf{A}_{12} | \mathbf{A}_{11} | \mathbf{A}_{10} | A 9 | A 8 | $\mathbf{A_7}$ | $\mathbf{A_6}$ | \mathbf{A}_5 | A 4 | \mathbf{A}_3 | $\mathbf{A_2}$ | \mathbf{A}_1 | $\mathbf{A_0}$ |
|--------|-------------|----------|-----------------|-------------------|-------------------|-------------------|-------------------|-------------------|-------------------|-------------------|------------|------------|----------------|----------------|----------------|------------|----------------|----------------|----------------|----------------|
| Start | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| Addres | | | | | | | | | | | | | | | | | | | | |
| S | | | | | | | | | | | | | | | | | | | | |
| End | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| Addres | | | | | | | | | | | | | | | | | | | | |
| S | | | | | | | | | | | | | | | | | | | | |

Data Segment starts at address location 00000_H and is of size 1KB.


Stack segment starts at address 00800_H and is also of size 1KB.

Now, let us consider ROM.

✓ ROM must house the code segment.

Starting address of ROM = $FE000_H$

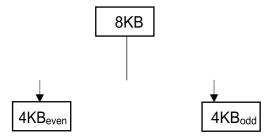System has 8KB ROM. So, Ending address of ROM = FFFFF_H.



$$\label{eq:even-bank-of-ROM} \begin{split} \textbf{Even Bank of ROM} &= FE000_H, FE002_H, FE004_H, FE006_{H, \dots}, FEFFE_{H.} \\ \textbf{Odd Bank of ROM} &= FE001_H, FE003_H, FE005_H, FE007_{H, \dots}, FEFFF_{H.} \\ \end{split}$$

| | A 19 | A ₁₈ | A ₁₇ | \mathbf{A}_{16} | A ₁₅ | A ₁₄ | \mathbf{A}_{13} | \mathbf{A}_{12} | \mathbf{A}_{11} | \mathbf{A}_{10} | A 9 | A ₈ | A_7 | A ₆ | \mathbf{A}_{5} | A 4 | \mathbf{A}_3 | $\mathbf{A_2}$ | $\mathbf{A_1}$ | $\mathbf{A_0}$ |
|----------------------|-------------|------------------------|-----------------|-------------------|------------------------|------------------------|-------------------|-------------------|-------------------|-------------------|------------|-----------------------|-------|-----------------------|------------------|------------|----------------|----------------|----------------|----------------|
| Start Addres s | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| End Addres s | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

The code begins at the address FF000_H.

The first address the processor sends out when it is switched on is FFFFO_H.

At this location, there is a jump instruction which takes the program control to the beginning of the code.

(C) IO BASED MEMORY MAPPING:

1.) 8253 Programmable Interval Timer

According to our problem statement, we need to check values from sensors every 2 seconds. For this we need a timer and hence we are using 8253. It is organized in the following way:

| | Address | A7 | A6 | A5 | A4 | А3 | A2 | A1 | A0 |
|---------|-----------------|----|----|----|----|----|----|----|----|
| Port A | $30_{\rm H}$ | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| Port B | $32_{\rm H}$ | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| Port C | 34 _H | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| Control | 36 _H | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| Reg. | | | | | | | | | |

2.)8255 Programmable Peripheral Interface




One 8255(Programmable Peripheral Interface) are used to communicate with other input and output devices. It is organized in the following manner

| | Addres | A7 | A6 | A5 | A4 | А3 | A2 | A1 | A0 |
|--------------|-----------------|----|----|----|----|----|----|----|----|
| | S | | | | | | | | |
| Port A | 00 _H | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| Port B | 02 _H | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| Port C | 04 _H | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| Control Reg. | 06 _H | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 |

(D)SENSOR:

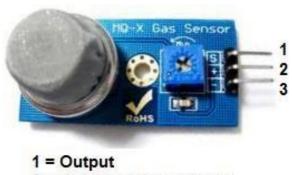MQ-2 Smoke Sensor circuit with built in Analog to digital convertor (with logic 1 as output in case of presence of smoke else logic 0 is the output)




2 = Vcc (positive voltage)

3 = Gnd

The 825 3 is u sed in Mod e 2 as a r at e c o un ter w here an in terrupt is giv en to the 8 086 m icroproce ssor every 2 s econds. On the interrupt the 8 086 c hecks for the values at the smoke detectors, that is if it is logic 1 or logic 0. On the basis of the following truth table the actions are taken

| SENSO R 1 | SENSO R 2 | ACTION TAKEN |
|--------------|--------------|---|
| 0 | 0 | Close d oor, v alves a nd windows |
| 0 | 1 | Close d oor, v alves a nd windows |
| 1 | 0 | Close d oor, v alves a nd windows |
| 1 | 1 | Open door, valves a nd windows |

FLOWCHART

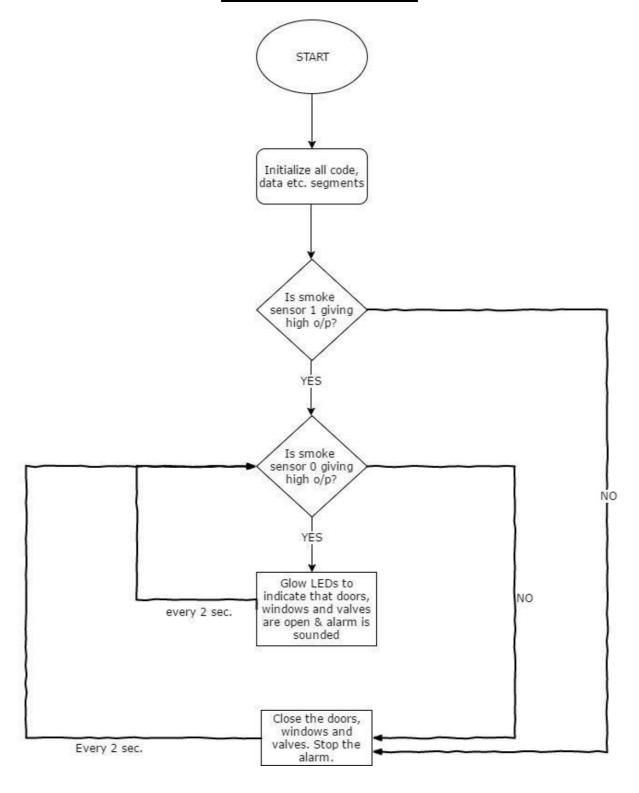

CODE

;The code is situated in the location ff000h #make_bin# #LOAD_SEGMENT=FFFFh# #LOAD_OFFSET=0000h# #CS=0000h# #IP=0000h# #DS=0000h# #ES=0000h# #SS=0000h# #SP=0800sh# #AX=0000h# #BX=0000h# #CX=0000h# #DX=0000h# #SI=0000h# #DI=0000h# #BP=0000h# ; add your code here jmp st1 db 1024 dup(0) ;main program st1: ;clear interrupt flags cli ; intializeds, es, ssto start of RAM mov ax,0000h mov ds,ax mov es,ax mov ss,ax sp,0800H mov ;intialise porta & b as input &portc as output

mov al,92h;10010010b


```
out 06h,al
;initialise counter mode 2 in 8253
    ;30h = address of count0 i.e. starting address for 8253
    ;count reqd = 5*10^6
    ;count0 stores 2500
   mov al,34h
   out 36h,al
   mov al,0C4h
   out 30h,al
    mov al,09h
    out 30h,al
    ;count1 stores 2000
   mov al,74h
   out 36h,al
   mov al,0D0h
   out 32h,al
    mov al,07h
   out 32h,al
    ;take input from smoke sensors
next: in al,00h
   mov bl,al
    ;check if both are on or not
   cmp bl,81h
   inz off
    ; open valves, doors and windows and sound alarm
glow:
        mov al,0C0h
   out 04h,al
   jmp over
    ; close valves, doors and windows
off:
                al,0FFh
        mov
    out
          04h,al
   jmp over
over:
    interupt generation using out of 8253 after every 2 seconds
   lea si,read
          ds:[256],si;vectornumber=40h=64d,solocationinIVT=64*4
mov
    =256 mov cx,cs
```

mov ds:[258],cx

```
;settheinterruptflags
sti
;infinite loop, will stop only powers switched off
jmp next


read proc near:
iret
read endp
```

CIRCUIT DIAGRAM

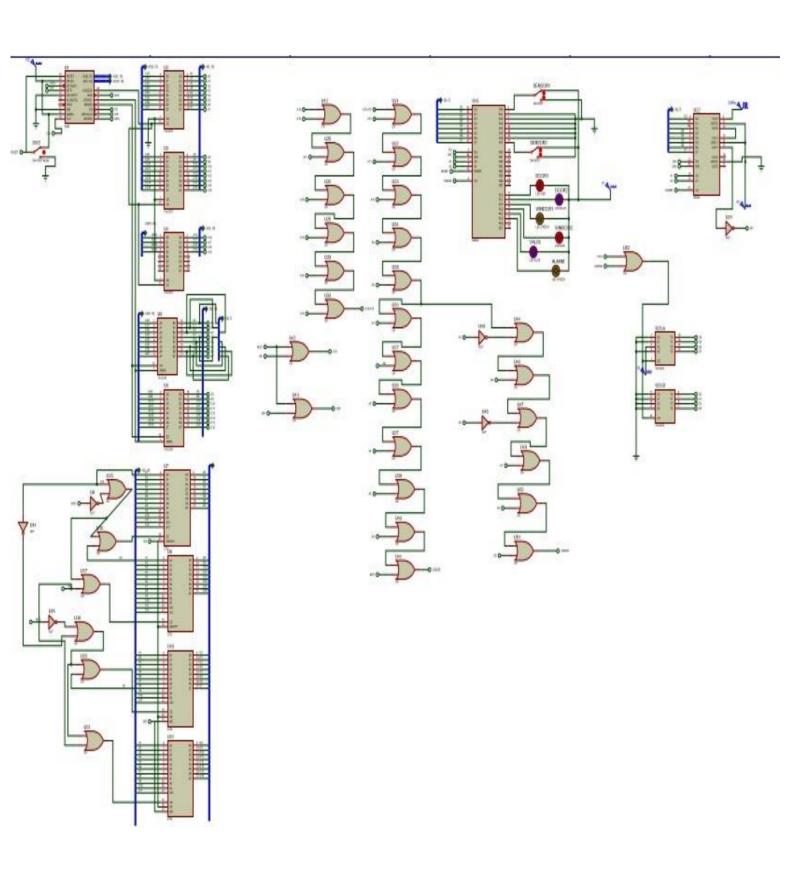

In the above circuit 8284 was used to generate the required clock at frequencies 5MHz and

2.5 MHz

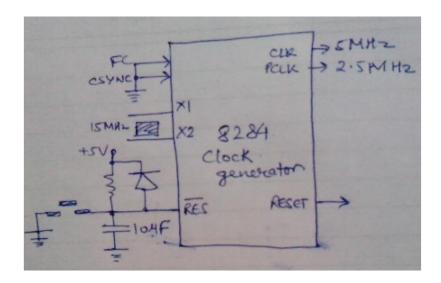

REFERENCES TO MANUALS USED

- > 8085/86
- > x86 processors (Intel processors book by Barey Brey)
- ➤ 2716_EPROM
- **>** 6116
- ▶ 8255
- ➤ adc0808-n (for understanding the concept of ADC, not used in project though)
- > SN74LS245
- > SN74LS373

All the above manuals were either searched on Internet or a vailable on E dx for student's reference.

For the smoke sensors, the below sites were referred

- http://www.learningaboutelectronics.com/Articles/MQ-2-s moke-sensor-circuit-with-arduino.php
- http://store.fut-electronics.com/products/smoke-sensor-module-mq2-digital-analog
- ht tp://www.nrdcentre.com/MQ2-Smoke-Sensor-Modulehttp://www.hw-group.com/products/sensors/index_en.html